

# **Voltage and Current Smoother for a 9 V battery**

**Team Spaklers**

**220235V - Ilukkumbura IMEIB**


**220495P- Priyanjana TPIM**

**220004M- Aashir MRM**

**220071M- Basith MNA**
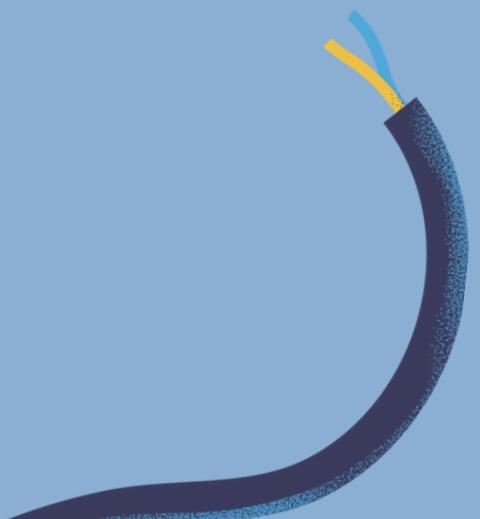
# Introduction

Even though batteries are a portable and easy power source, they can occasionally provide varying current and voltage because of a number of variables, including ambient influences, load variations, and battery health. In electronic applications, these variations may result in noise, instability, and decreased efficiency. A smoothing circuit is used to reduce voltage fluctuations and steady the voltage in order to solve the problem.



## **What is a DC Current and Voltage Smoother?**


A DC Current and Voltage Smoother is a device designed to stabilize both current and voltage in direct current (DC) circuits. It ensures that the voltage and current delivered to connected components remain constant, even if there are fluctuations in the input power supply.

## **Why is it Important?**

- Ensures stable power delivery to prevent malfunction or damage.
- Reduces noise in systems like audio or analog circuits.
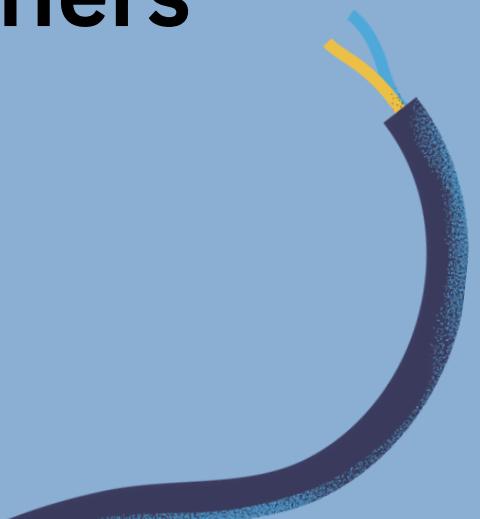
## **Key Applications:**

- Battery-operated devices
- Sensitive electronics like microcontrollers, sensors, and amplifiers





# Our Specifications




## Current Smoother

- Input Voltage : 9v - 7V
- Output Current : 50mA - 53 mA
- Load Resistance : 0-75ohm

## Voltage Smoother


- Input Voltage : 9v - 7V
- Output Voltage : 7V
- Min Load Resistance : 470ohm

# Current Smoother

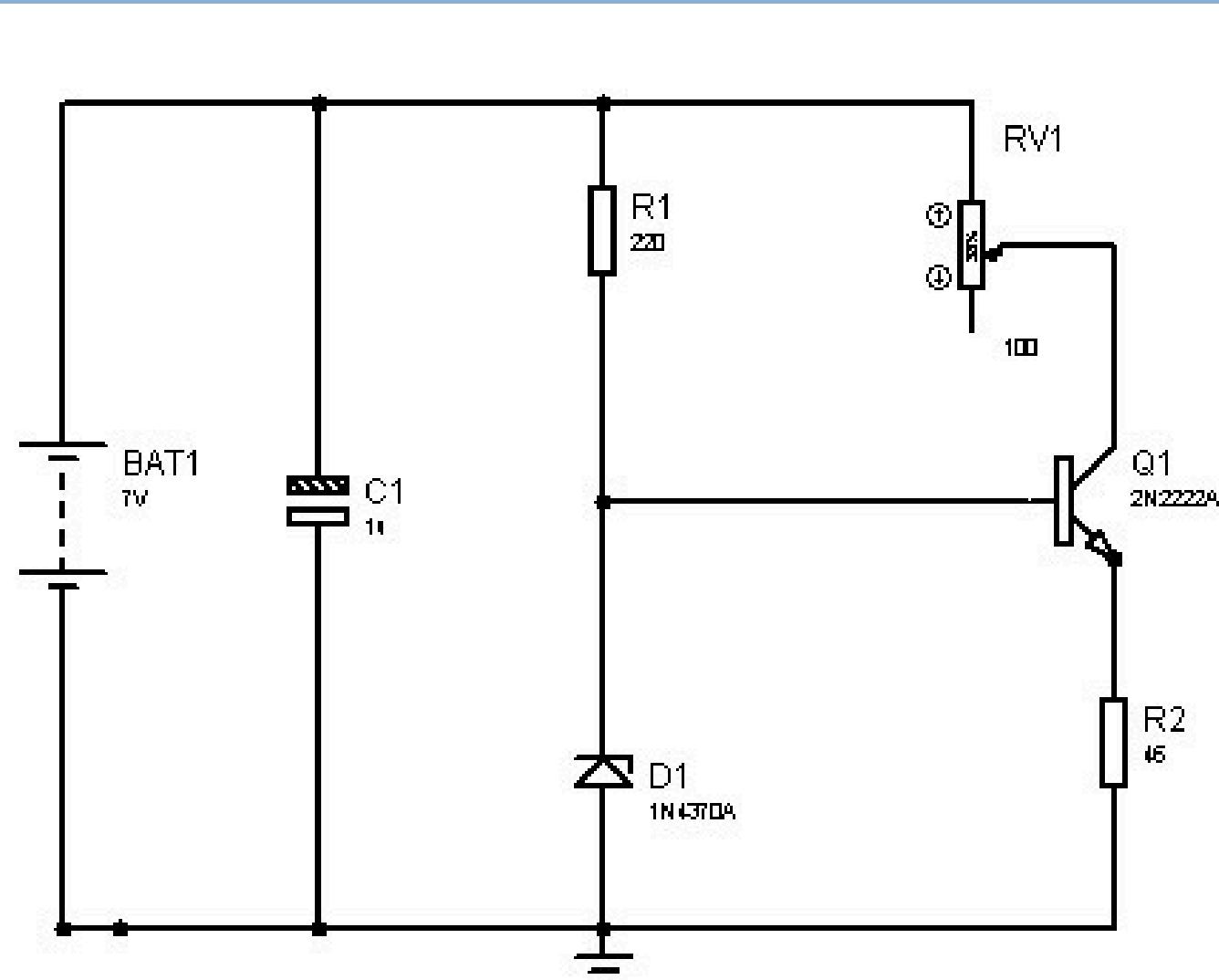


- A constant  $V_E$  is Given by zenor diode.
- Hence the  $I_b$  becomes Constant
- As  $I_b$  is constant, the collector current ( $I_C$ ) also remains constant.
- The transistor (Q1) maintains a steady current through the resistor (R2).
- The potentiometer (RV1) is used to demonstrate variable Load Resistance

# Testing

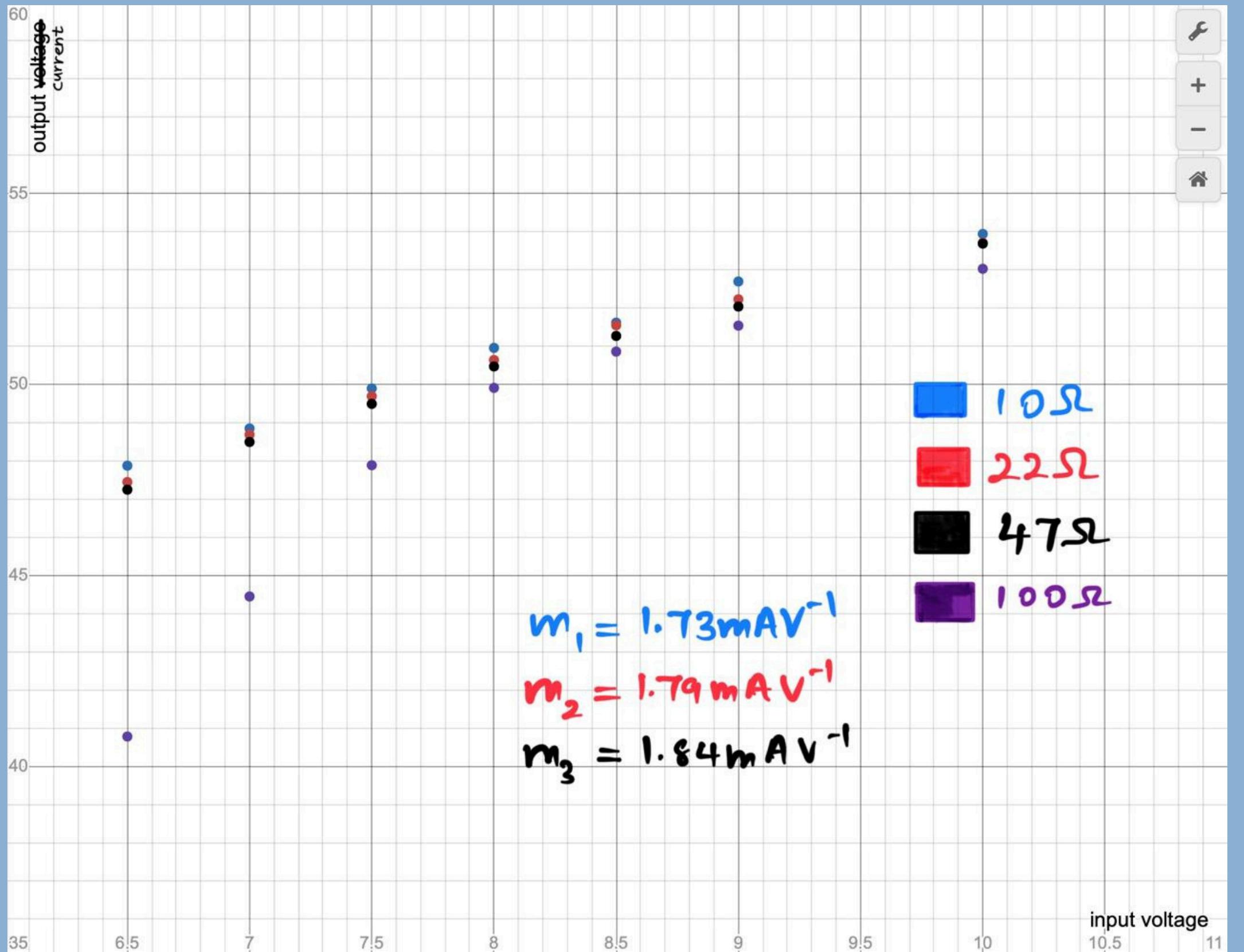

# Voltage Smoother

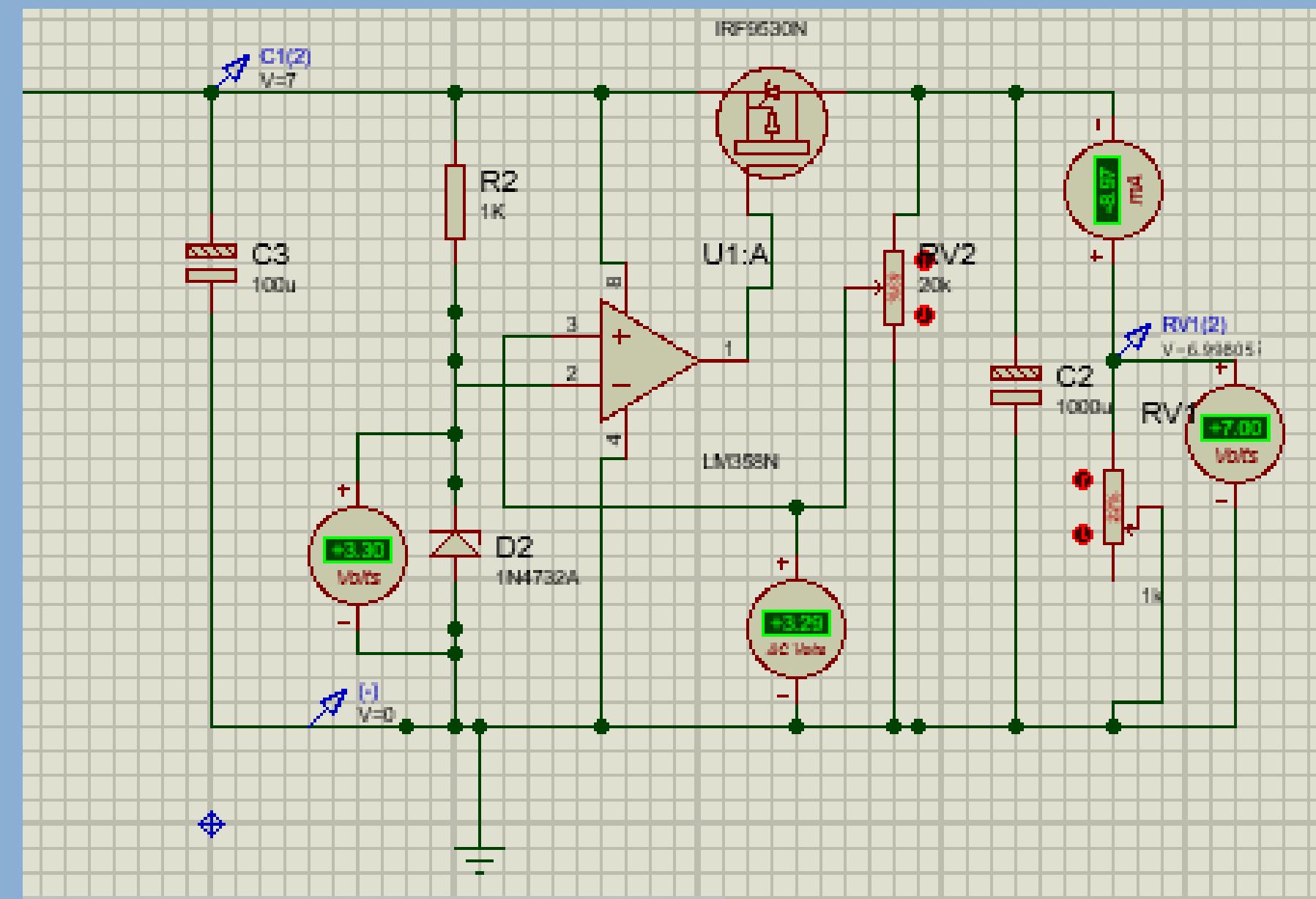

## Error Amplifier:

- Compares a fraction of the output voltage (via a resistor divider network) to a reference voltage(Zener Voltage).
- Produces an error signal that adjusts the gate voltage of the PMOS to regulate the output voltage.




## PMOS Pass Element:

- Acts as the main regulating component, controlling the flow of current from VIN to VOUT.
- The PMOS transistor operates in the linear region to regulate voltage.
- Since a PMOS transistor is used, the dropout voltage (difference between VIN and VOUT)

## Stability:

- The circuit may include capacitors (not shown in this basic diagram) for stability, ensuring that the output voltage is smooth and free from oscillations.




# Testing

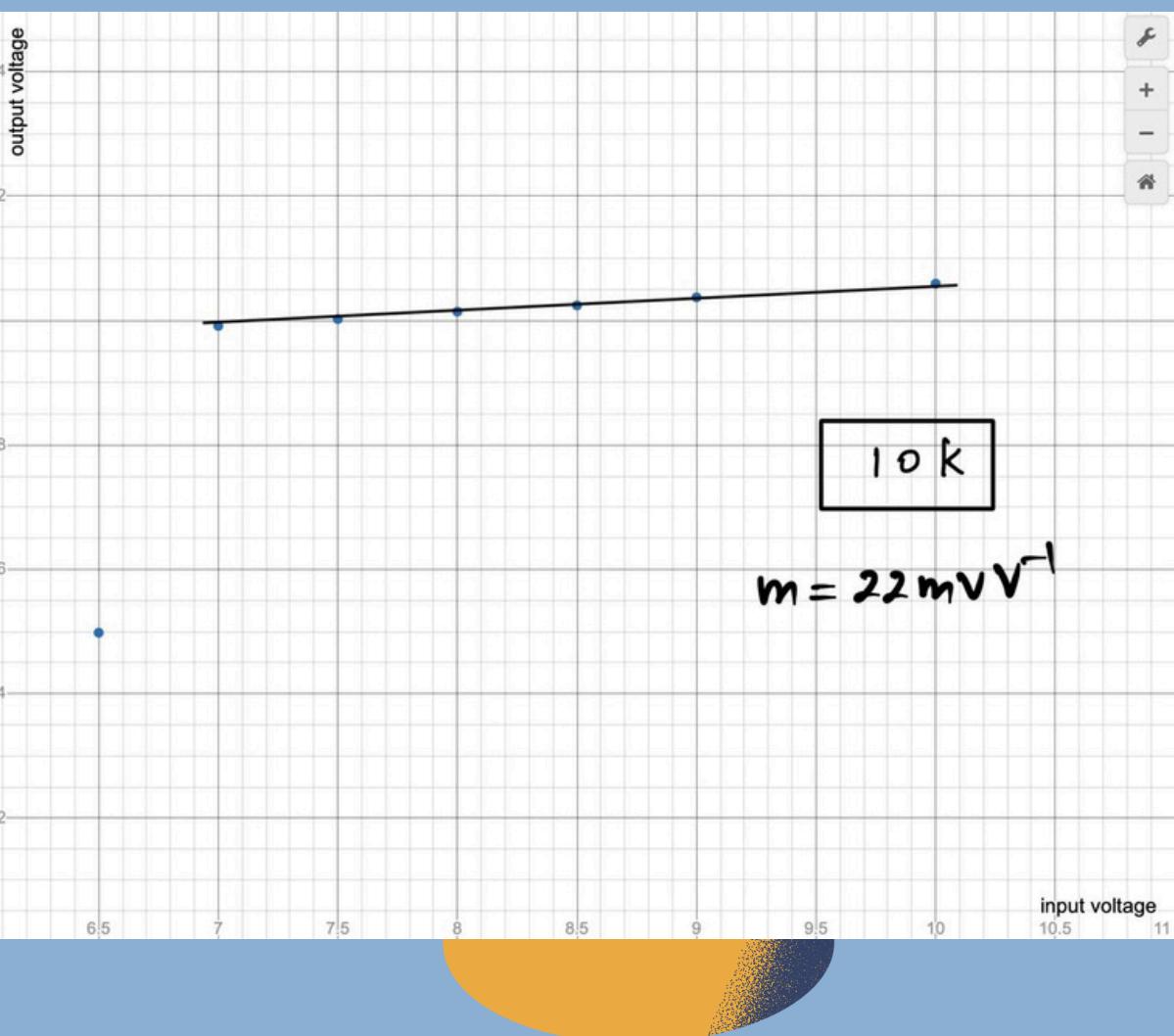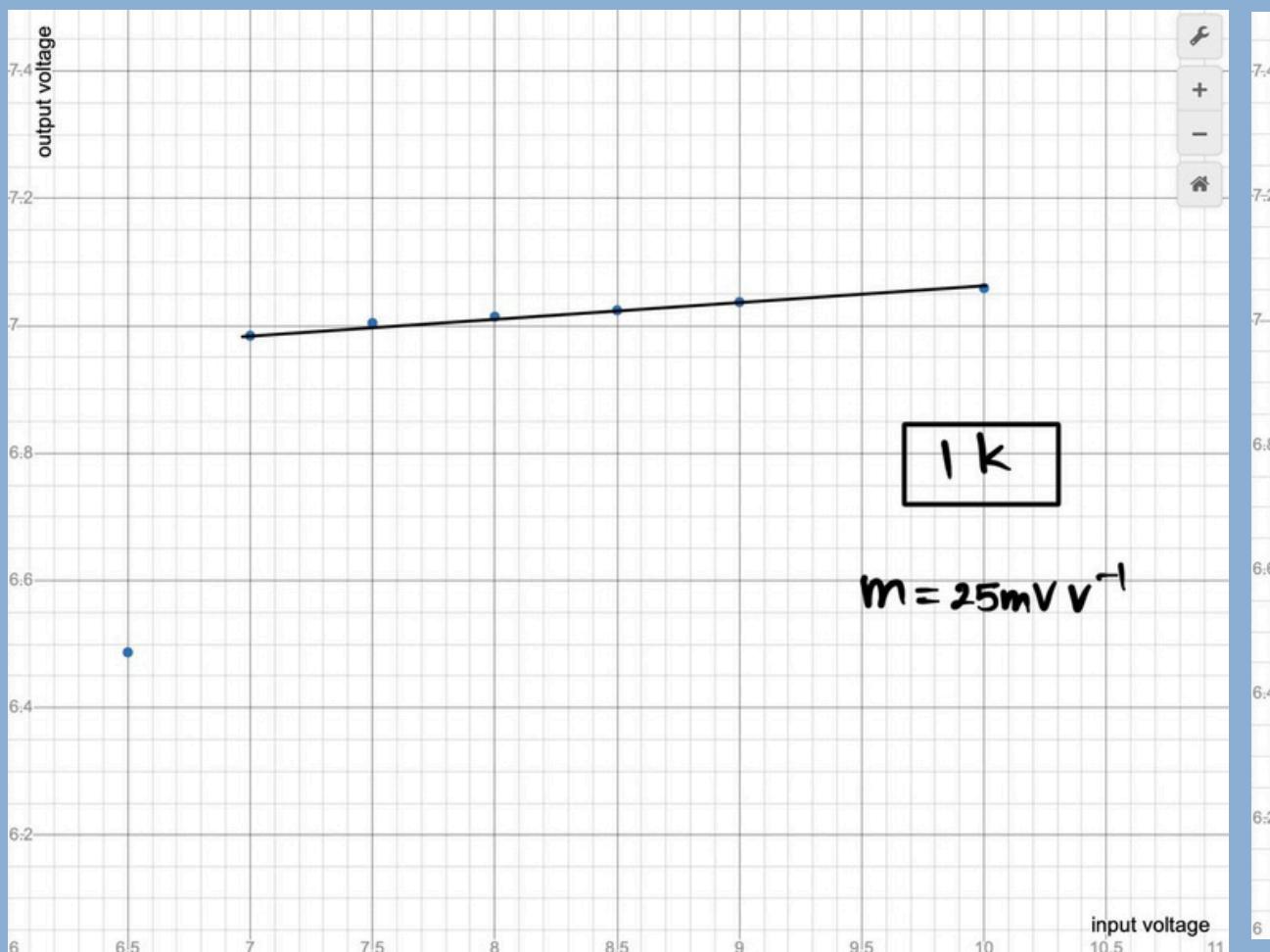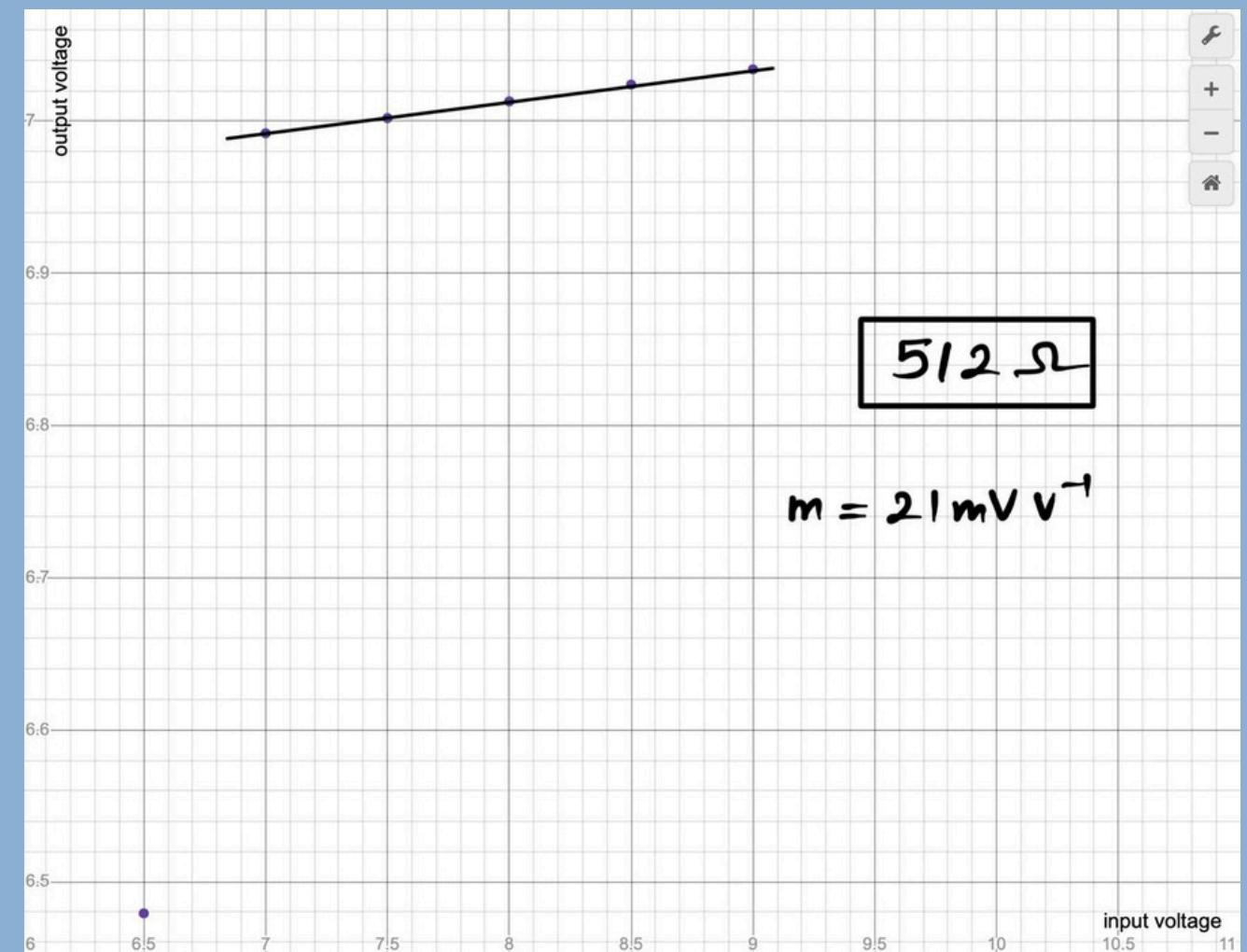




- IFN9530N MOSFET - low dropout voltage , Good for low-voltage operation
- LM358N op-amp - Single Supply: 3V to 32V , Draws 0.5 mA per amplifier, which is relatively low. Inexpensive and widely available but noise is relatively high.  $50 \mu\text{V/V}$  - PSRR , 70 dB -CMRR , input offset voltage 2 mV
- 2N2222A Transistor - Can handle up to 800 mA ,  $V_{ce(\text{sat})}$  is low 2N2222 (NPN) or BC547 (NPN) for low current; TIP31 (NPN) or TIP32 (PNP) for higher current.



# PCB design

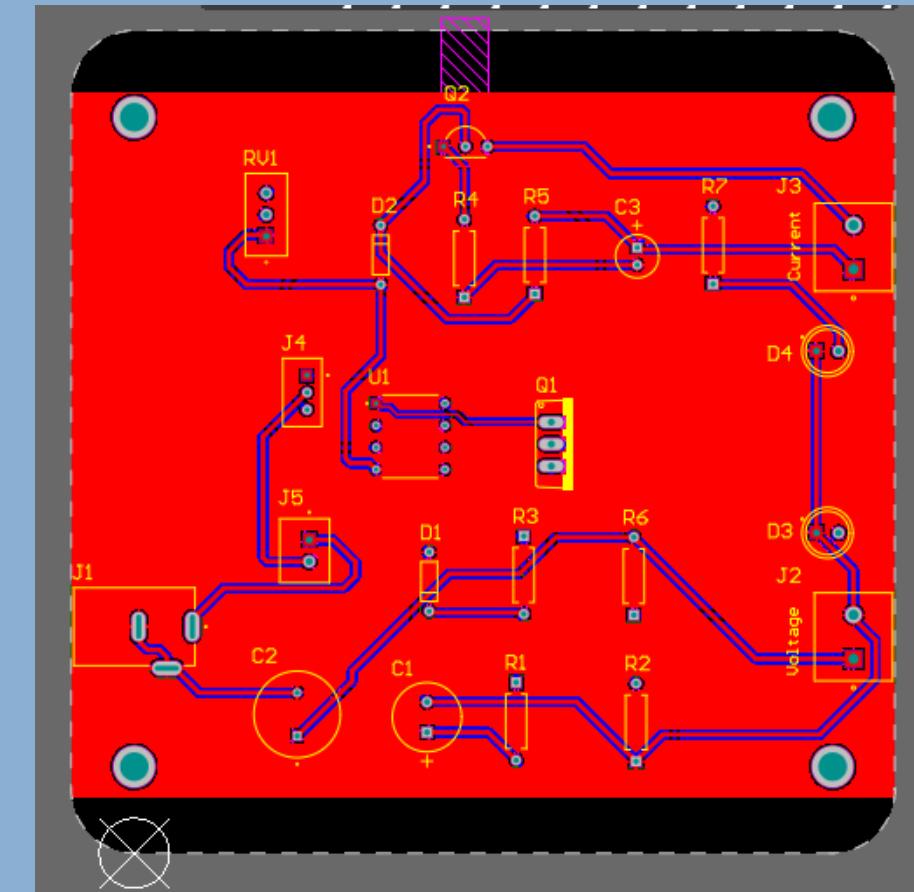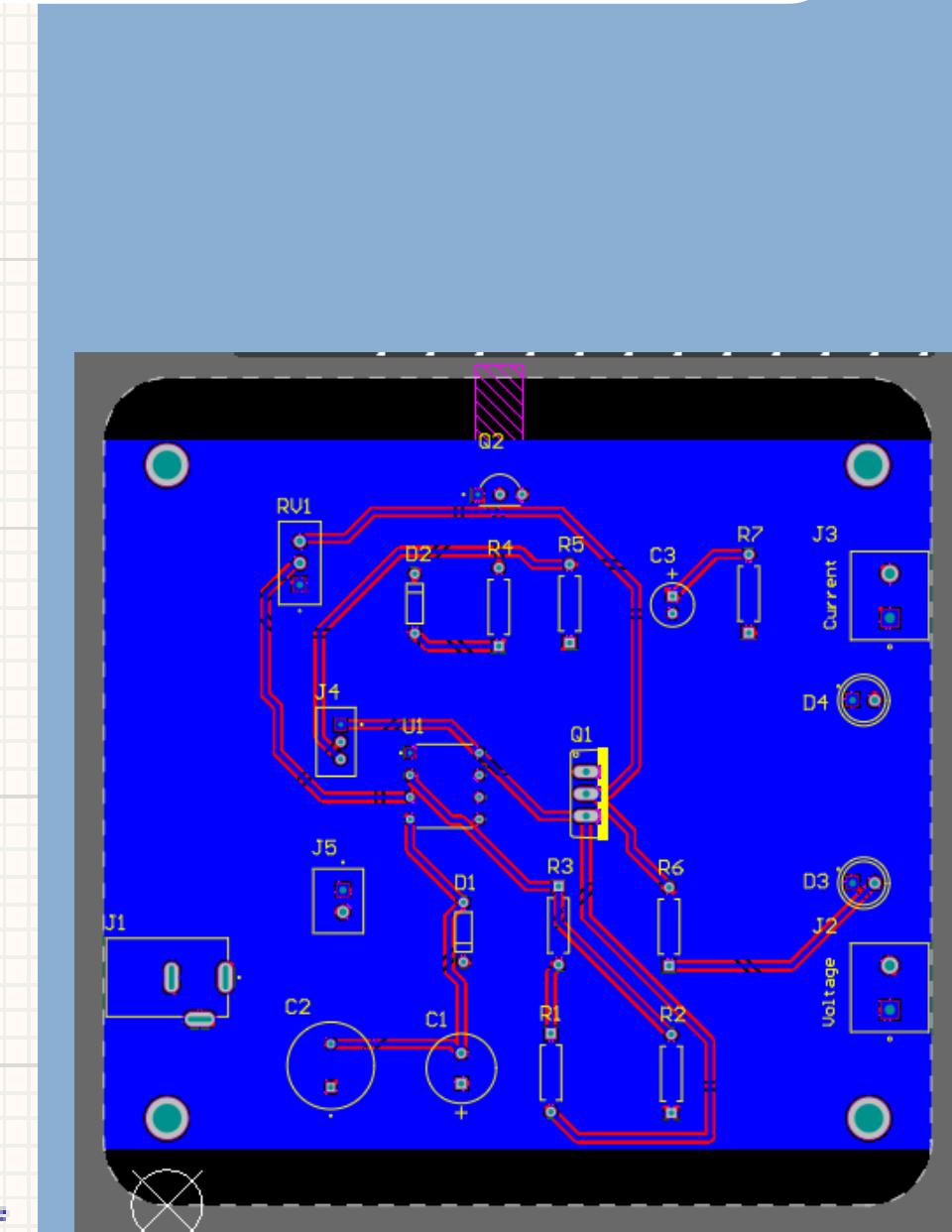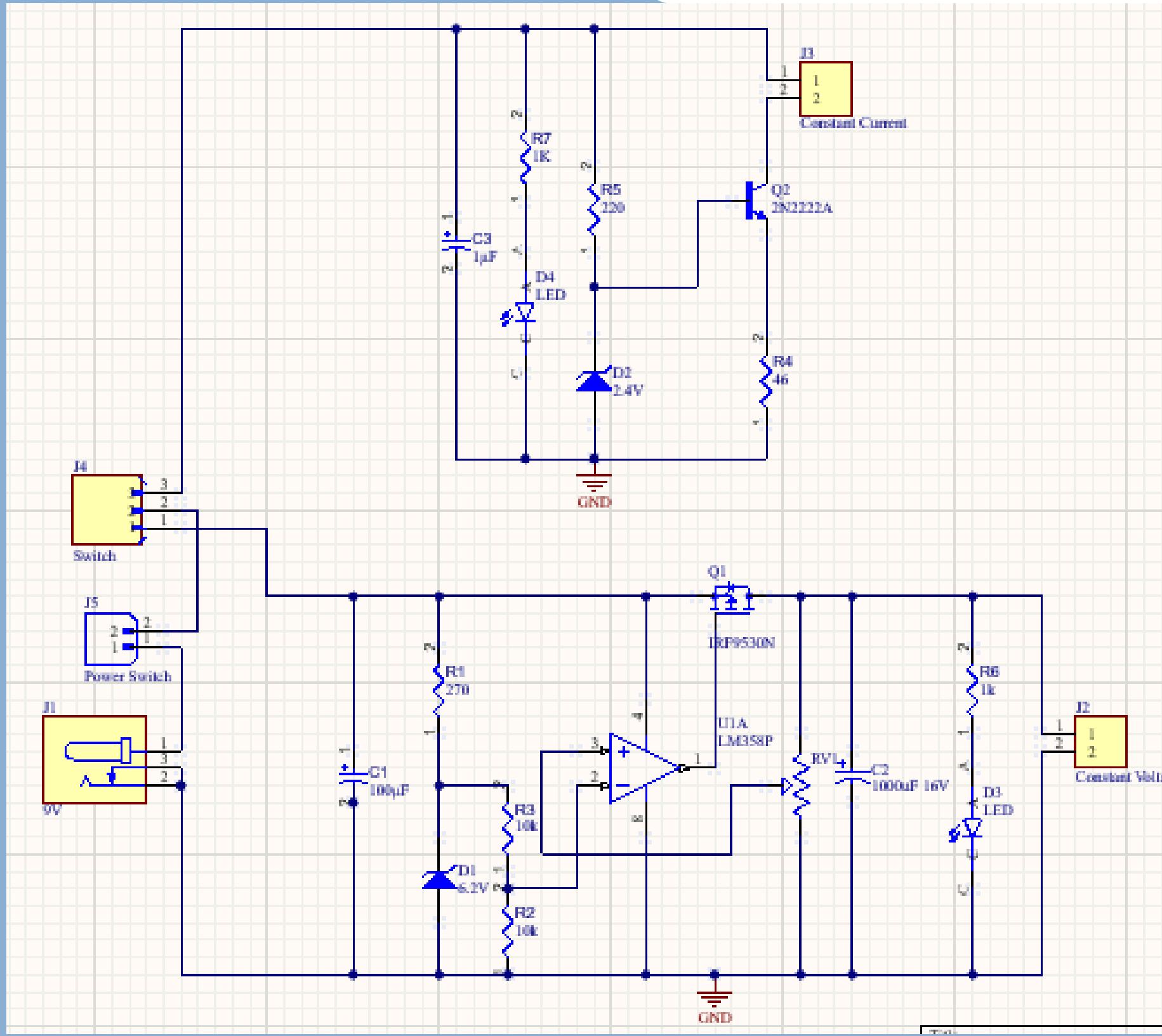

# Enclosure design

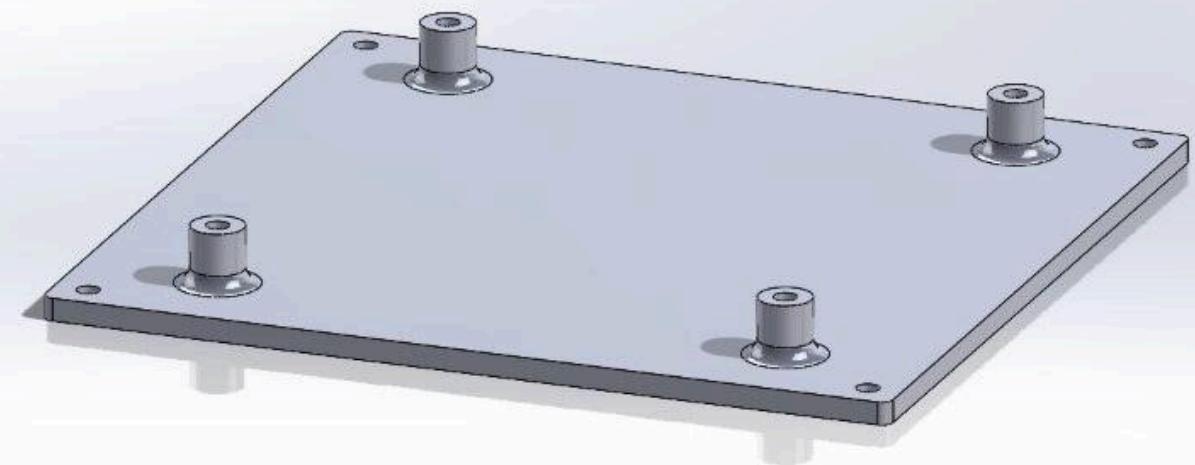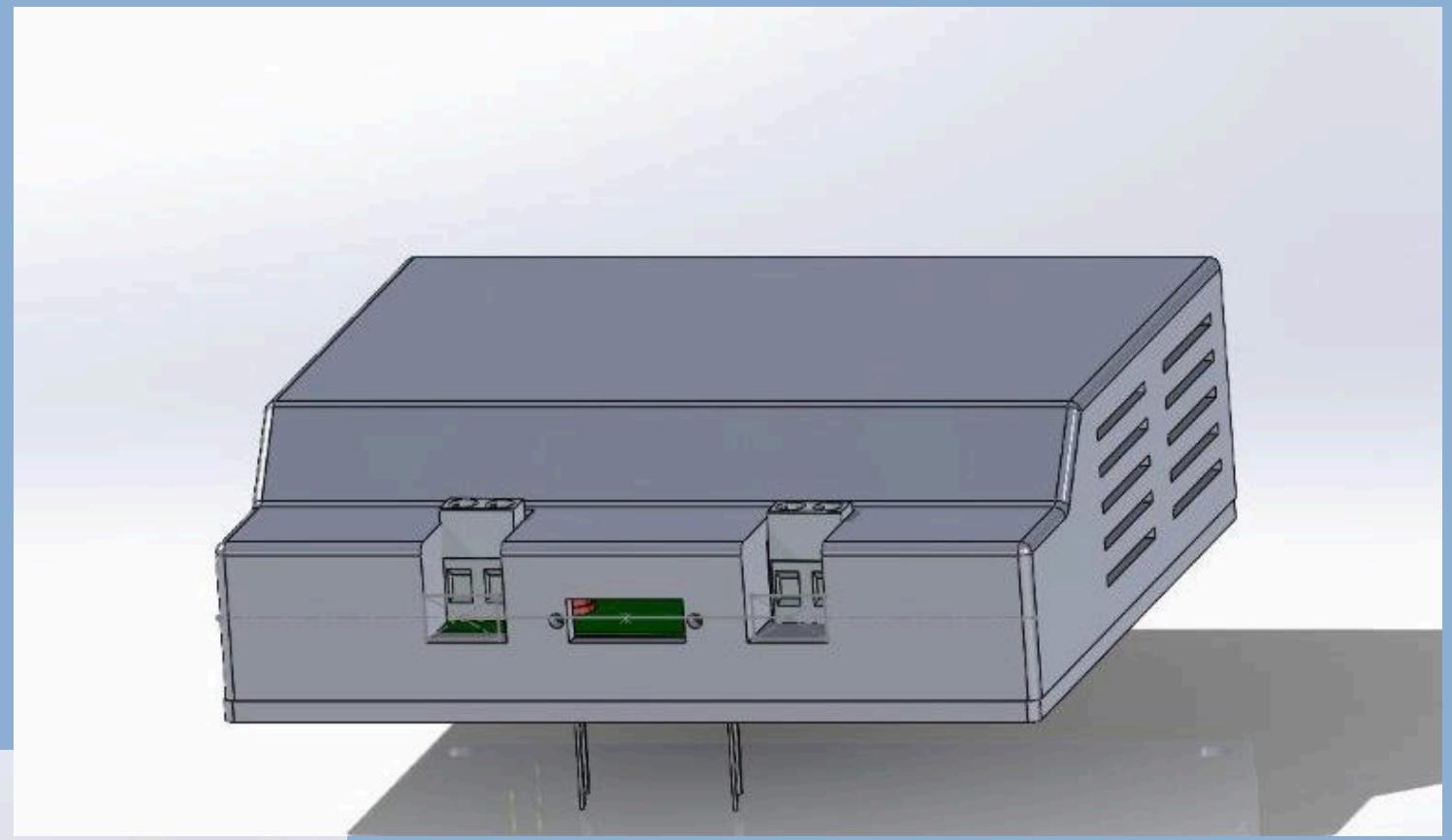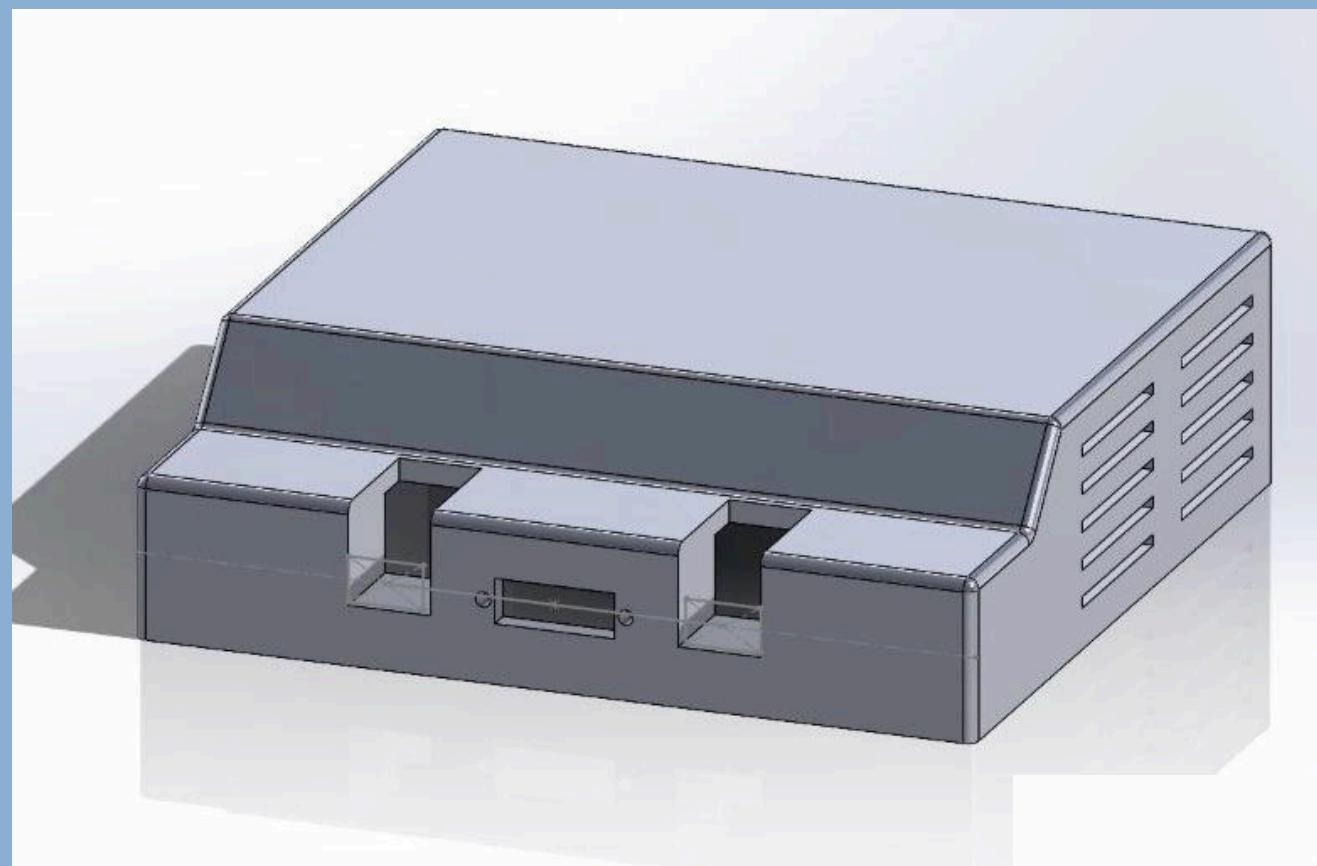

# Task Allocation

Ilukkumbura IMEIB - Constant voltage circuit design and simulation.

Priyanjana TPIM - PCB design and circuit testing

Aashir MRM - Constant current circuit design and simulation

Basith MNA - Encloser design and circuit testing

# **Q and A**

**Thank You**